

Chapter 10: Synchronous Circuits

Computer Structure & Intro. to Digital Computers

Dr. Guy Even

Tel-Aviv Univ.



Goals

- define synchronous circuits.
- analyze timing (start with simple case...).
- define: timing constraints.
- find out if timing constraints are feasible.
- define: minimum clock period.
- algorithm: check if timing constraints are feasible.
- algorithm: compute minimum clock period.

Striping flip-flops away

- C - a circuit composed of combinational gates, nets, and flip-flops with a clock net called `CLK`.
- C' - a circuit obtained from C by:
 1. deleting the `CLK` net,
 2. deleting the input gate that feeds the `CLK` net, and
 3. replacing each flip-flop with an output gate (instead of the port D) and an input gate (instead of the port Q).

Striping flip-flops away - example

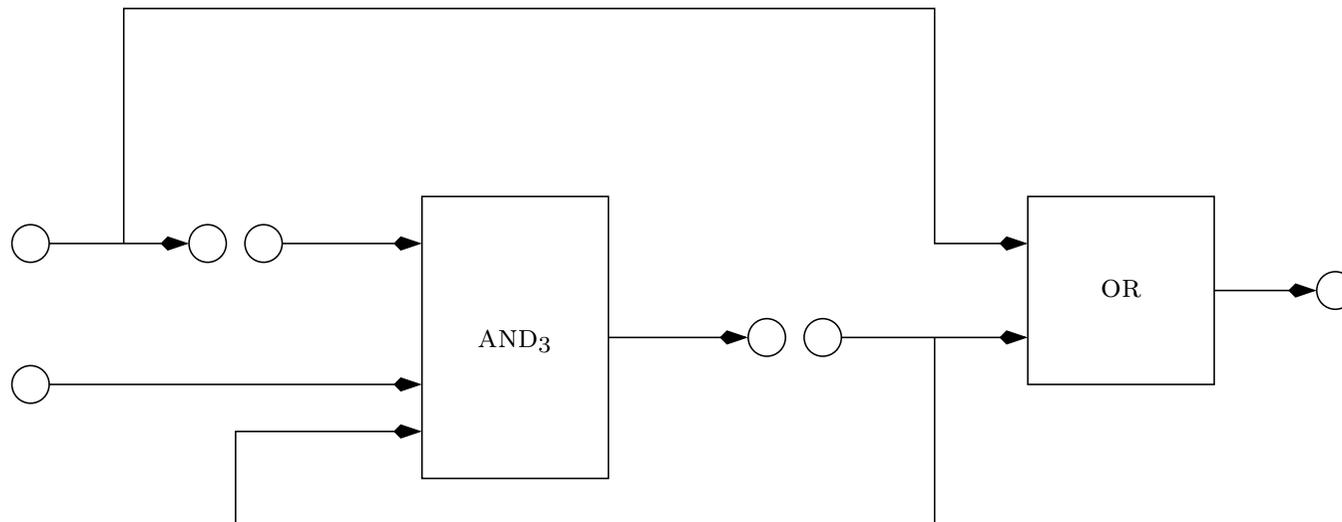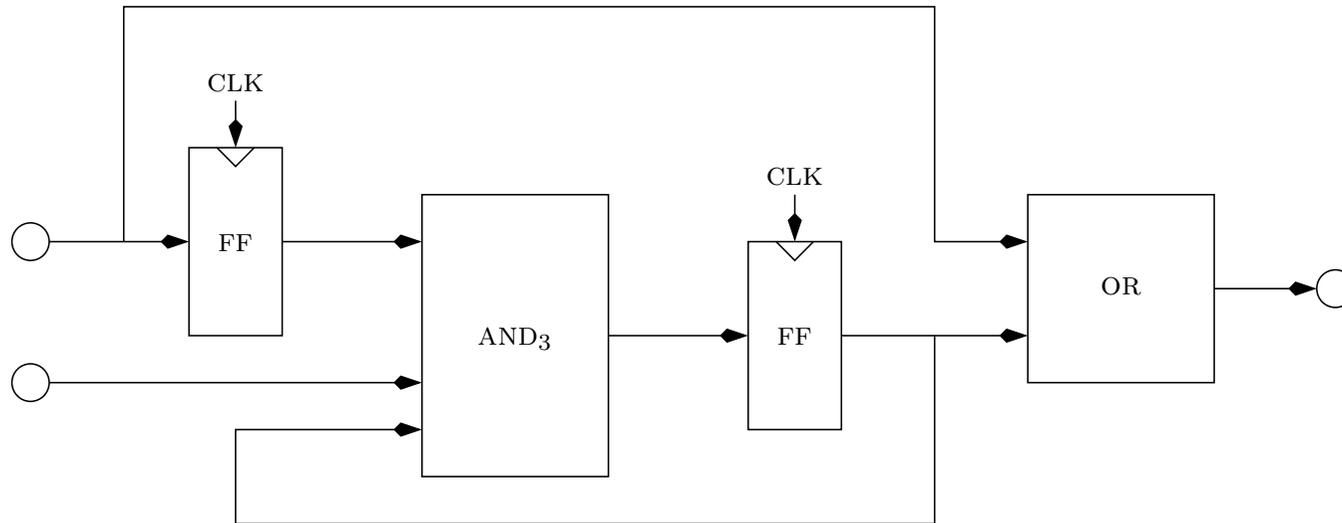


Definition: Synchronous Circuit

A **synchronous circuit** is a circuit C composed of combinational gates, nets, and flip-flops that satisfies the following conditions:

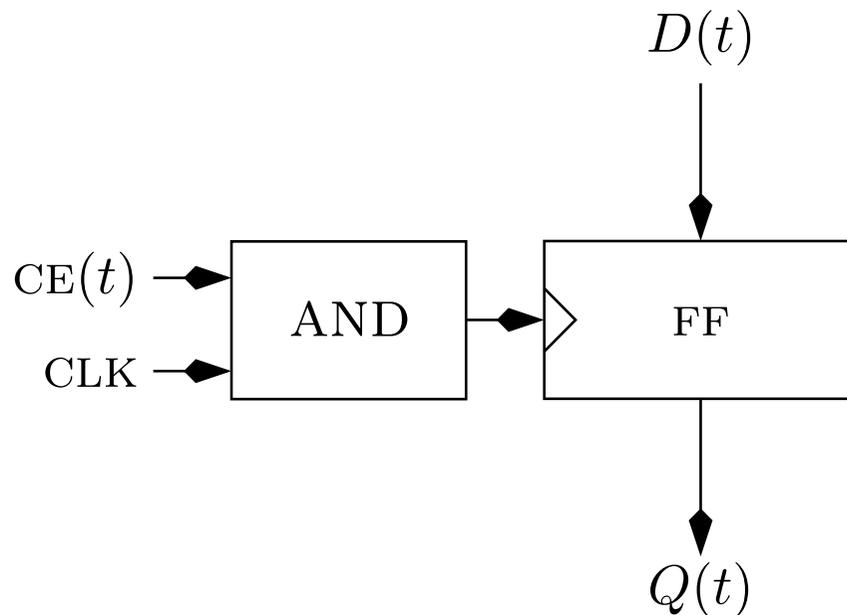1. There is a net called CLK that carries a clock signal.
2. The CLK net is fed by an input gate.
3. The set of ports that are fed by the CLK net equals the set of clock-inputs of the flip-flops.
4. The circuit C' obtained from C by stripping away flip-flops is combinational.


remarks on the definition of synchronous circuits

- CLK connected to all the clock-ports of flip-flops and only to them.
- We already saw that a “bad example” in which CLK feeds a gate:





remarks on the definition of synchronous circuits

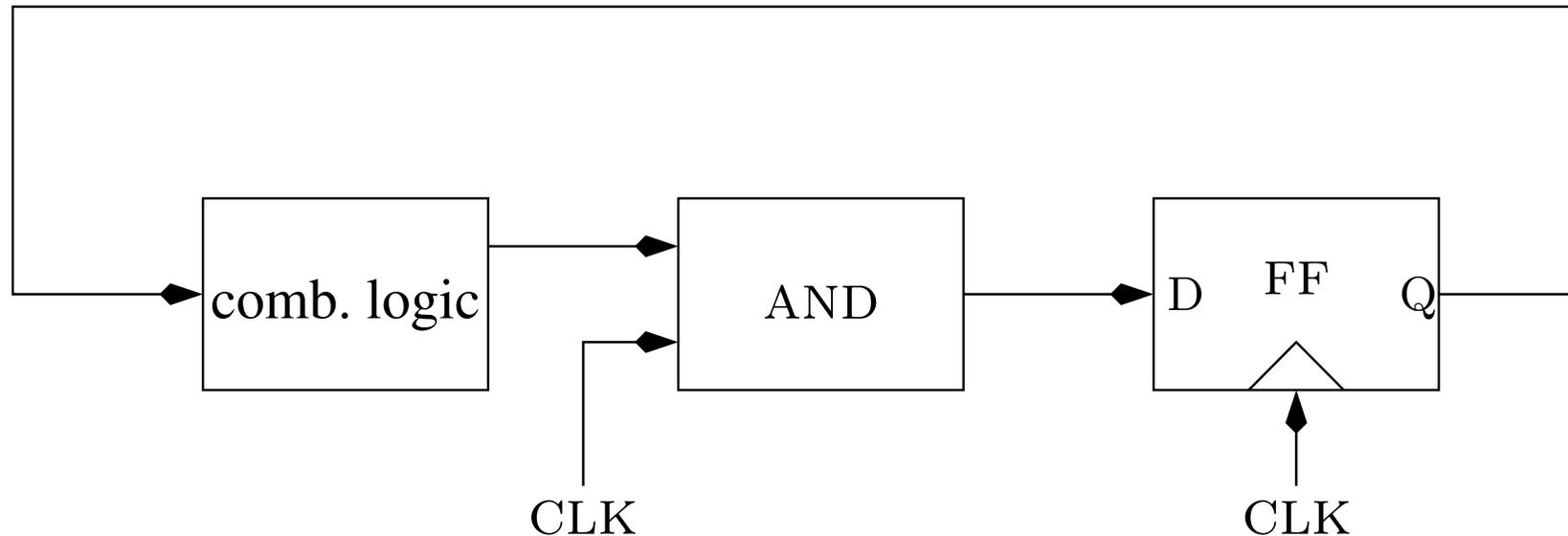Question: What is required so that the D -port is stable during the critical segment in this “bad example”:



back to the first example

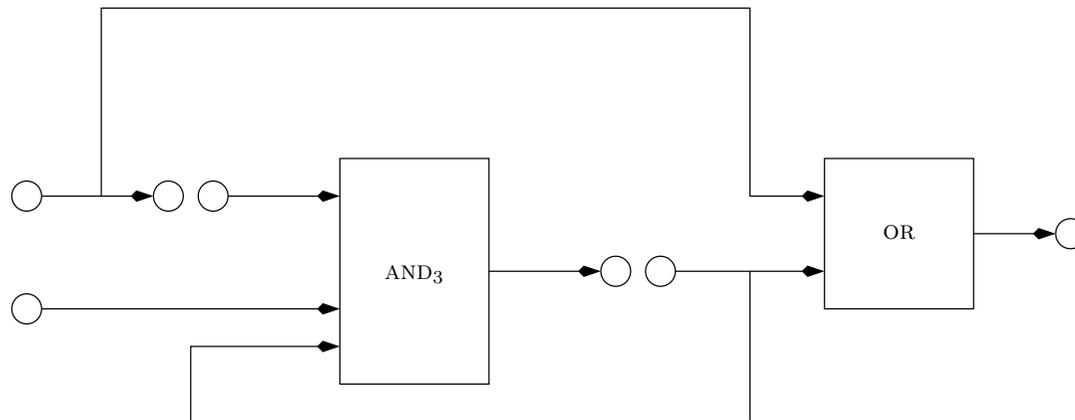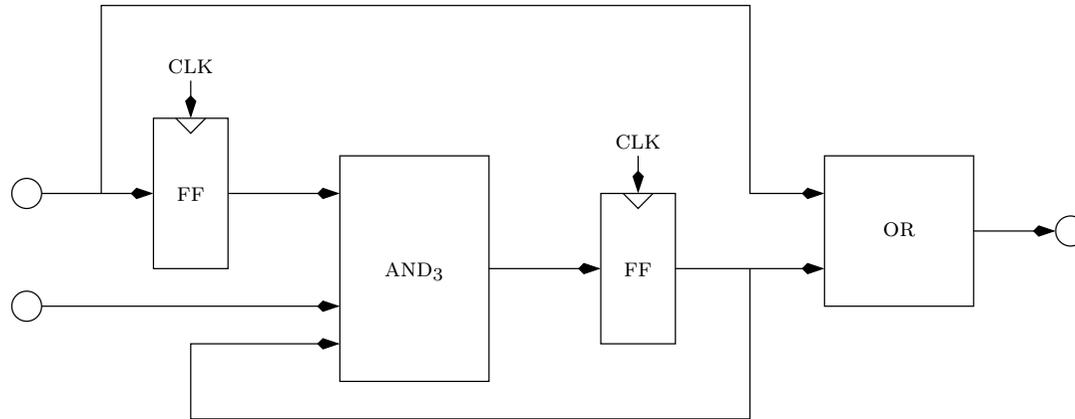

Question: Is this a synchronous circuit?


Recognizing a synchronous circuit

Question: Suggest an efficient algorithm that decides if a given circuit is synchronous.

A **synchronous circuit** is a circuit C composed of combinational gates, nets, and flip-flops that satisfies the following conditions:

1. There is a net called CLK that carries a clock signal.
2. The CLK net is fed by an input gate.
3. The set of ports that are fed by the CLK net equals the set of clock-inputs of the flip-flops.
4. The circuit C' obtained from C by stripping away flip-flops is combinational.

Synchronous Circuits: canonic form

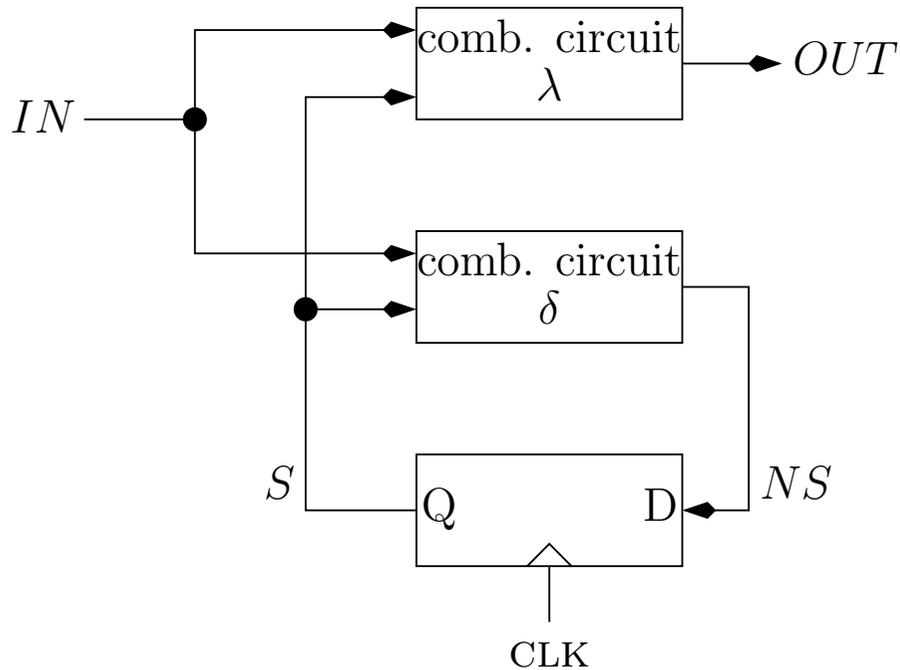


Transform a synchronous to canonic form:

- gather the flip-flops into one group.
- duplicate the combinational circuits to separate between output and next-state.

Stability Interval

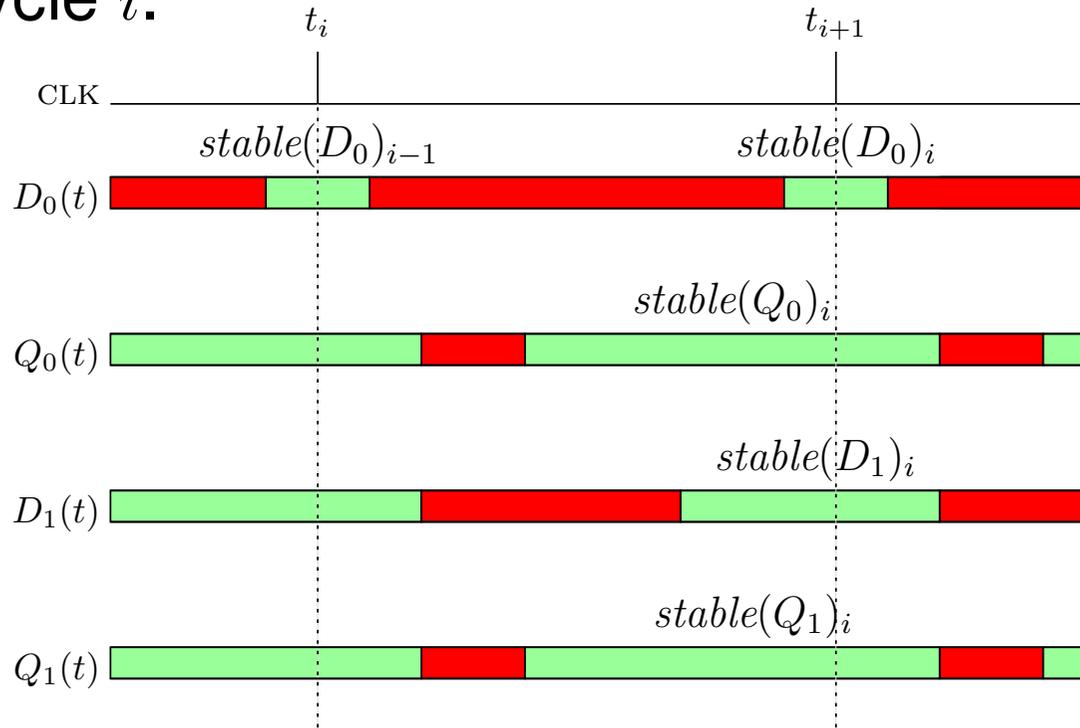- **stability interval** of signal X - interval during which X is stable.
- **$stable(X)_i$** - stability interval of X corresponding to clock cycle i .



Timing analysis: the canonic form

Plan:

- Define timing constraints for *IN* and *OUT*.
- Define timing constraints for *S* and *NS*.
- Find sufficient conditions so that timing constraints are feasible.
- Define minimum clock period.
- Infer functionality from syntax.

Input/output timing constraints

- The input/output timing constraints formulate the timing interface between the the circuit and the “external world”.
- Input timing constraint - tells us when the input is **guaranteed** to be stable.
- Output timing constraint - tells us when the circuit’s output is **required** to be stable.
- Usually the external world is also a synchronous circuit.
⇒ IN is an output of another synchronous circuit, and OUT is an input of another synchronous circuit.

Input timing constraint

The timing constraint corresponding to IN is defined by two parameters: $pd(IN) > cont(IN)$ as follows.

$$\forall i : [t_i + pd(IN), t_{i+1} + cont(IN)] \subseteq stable(IN)_i.$$

Remarks:

- t_i - denotes the starting time of the i th clock period.
- Why do we require that $pd(IN) > cont(IN)$?
If $pd(IN) \leq cont(IN)$, then the stability intervals $stable(IN)_i$ and $stable(IN)_{i+1}$ overlap. This means that IN is always stable, which is obviously not an interesting case.

Output timing constraint

The timing constraint corresponding to OUT is defined by two parameters: $setup(OUT)$ and $hold(OUT)$ as follows.

$$\forall i : [t_{i+1} - setup(OUT), t_{i+1} + hold(OUT)] \subseteq stable(OUT)_i.$$

Remark: Note that that timing constraint of OUT is given relative to the end of the i th cycle (i.e. t_{i+1}).

Remarks

- asymmetry in the terminology regarding IN and OUT . The parameters associated with IN are $pd(IN)$ and $cont(IN)$, whereas the parameters associated with OUT are $setup(OUT)$ and $hold(OUT)$.
- this is not very aesthetic if OUT is itself an input to another synchronous circuit.
- useful to regard IN as an output of a flip-flop and OUT as an input of a flip-flop (even if they are not).

Timing constraint of NS

NS is stable during the critical segments. Namely,

$$\forall i \geq 0 : C_{i+1} \subseteq \mathit{stable}(NS)_i.$$

Remark: Note that, as in the case of the output signal, the timing constraint of NS corresponding to clock cycle i is relative to the end of the i th clock cycle (i.e. the critical segment C_{i+1}).

Remark: If NS satisfies its timing constraint for i , then S satisfies:

$$[t_{i+1} + t_{pd}, t_{i+2} + t_{cont}] \subseteq \mathit{stable}(S)_{i+1}.$$

Stability Intervals of *OUT* & *NS*

- We associate a contamination delay $cont(x)$ and a propagation delay $pd(x)$ with each combinational circuit x .
- If $[t_i + t_{pd}, t_{i+1} + t_{cont}] \subseteq stable(S)_i$, then the stability intervals of the signals *OUT* and *NS* satisfy:

$$[t_i + \max\{t_{pd}, pd(IN)\} + pd(\lambda), t_{i+1} + \min\{t_{cont}, cont(IN)\} + cont(\lambda)] \\ \subseteq stable(OUT)_i$$

$$[t_i + \max\{t_{pd}, pd(IN)\} + pd(\delta), t_{i+1} + \min\{t_{cont}, cont(IN)\} + cont(\delta)] \\ \subseteq stable(NS)_i.$$

Sufficient conditions: *OUT*

Claim: If

$$\begin{aligned} [t_i + t_{pd}, t_{i+1} + t_{cont}] &\subseteq \mathbf{stable}(S)_i \\ \max\{t_{pd}, \mathbf{pd}(IN)\} + pd(\lambda) + \mathbf{setup}(OUT) &\leq t_{i+1} - t_i \\ \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\lambda) &\geq \mathbf{hold}(OUT), \end{aligned}$$

then

$$[t_{i+1} - \mathbf{setup}(OUT), t_{i+1} + \mathbf{hold}(OUT)] \subseteq \mathbf{stable}(OUT)_i.$$

Proof: stability interval of *OUT* satisfies:

$$\begin{aligned} [t_i + \max\{t_{pd}, \mathbf{pd}(IN)\} + pd(\lambda), t_{i+1} + \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\lambda)] \\ \subseteq \mathbf{stable}(OUT)_i \end{aligned}$$

Sufficient conditions: NS

Claim: If

$$[t_i + t_{pd}, t_{i+1} + t_{cont}] \subseteq \mathbf{stable}(S)_i$$

$$\max\{t_{pd}, \mathbf{pd}(IN)\} + \mathbf{pd}(\delta) + t_{su} \leq t_{i+1} - t_i$$

$$t_{hold} \leq \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\delta),$$

then the signal NS is stable during the critical segment

C_{i+1} .

Proof: stability interval of NS satisfies:

$$[t_i + \max\{t_{pd}, \mathbf{pd}(IN)\} + \mathbf{pd}(\delta), t_{i+1} + \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\delta)] \\ \subseteq \mathbf{stable}(NS)_i.$$

□

Timing constraints for $i \geq 0$

CORO: If 4 conditions hold and

$$[t_0 + t_{pd}, t_1 + t_{cont}] \subseteq \mathit{stable}(S)_0,$$

then

1. timing constraints of NS and OUT hold wrt every $i \geq 0$,
2. $\forall i \geq 0 : [t_i + t_{pd}, t_{i+1} + t_{cont}] \subseteq \mathit{stable}(S)_i$.

Proof: Induction on i .

- **Basis:** part (1) follows from sufficient conditions for OUT and NS .
- **Step:** NS is stable during $C_{i+1} \Rightarrow$ part (2).
- \Rightarrow part(1).

□

Simplifying the conditions

- Our goal is to simplify the conditions in the 2 Claims.
- Prefer: lower bounds on the clock period.
- \Rightarrow well defined functionality provided that the clock period is large enough.
- We discuss each of the 4 conditions (2 per claim).

$$\max\{t_{pd}, \mathbf{pd}(IN)\} + pd(\lambda) + \mathbf{setup}(OUT) \leq t_{i+1} - t_i$$

- condition is a lower bound on $\varphi(\text{CLK})$. Great.

$$\min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\lambda) \geq \mathbf{hold}(OUT)$$

- condition may not hold \Rightarrow serious problem that can lead to failure to meet the timing constraint of OUT ...
- Hope: under reasonable circumstances, condition does hold. Why?
 - Suppose IN is the output of a combinational circuit, all the inputs of which are outputs of flip-flops.
 - Assume that all the flip-flops are identical.
 - It follows that $\mathbf{cont}(IN) \geq t_{cont}$.
 - By definition: $\mathbf{cont}(\lambda) \geq 0$.
 - $\Rightarrow \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\lambda) \geq t_{cont}$.
 - Suppose OUT feeds a combinational circuit that feeds a flip-flop.
 - Hence $\mathbf{hold}(OUT) \leq t_{hold}$.
 - $t_{hold} < t_{cont} \Rightarrow$ condition holds.

$$\max\{t_{pd}, \mathbf{pd}(IN)\} + \mathbf{pd}(\delta) + t_{su} \leq t_{i+1} - t_i$$

- condition is a lower bound on $\varphi(\text{CLK})$. Great.

$$t_{hold} \leq \min\{t_{cont}, \mathbf{cont}(IN)\} + \mathbf{cont}(\delta)$$

- As before, if $\mathbf{cont}(IN) \geq t_{cont}$, the condition holds!

Conclusion

Claim: Assume that $cont(IN) \geq t_{cont}$ and $hold(OUT) \leq t_{hold}$.
If

$$[t_0 + t_{pd}, t_1 + t_{cont}] \subseteq \mathit{stable}(S)_0,$$

$$\varphi(\text{CLK}) \geq \max\{t_{pd}, \mathit{pd}(IN)\} + \max\{\mathit{pd}(\lambda), \mathit{pd}(\delta)\} + t_{su},$$

then

1. timing constraints of NS and OUT hold wrt every $i \geq 0$,
2. $\forall i \geq 0 : [t_i + t_{pd}, t_{i+1} + t_{cont}] \subseteq \mathit{stable}(S)_i$.

Under reasonable assumptions, all we need is **initialization** and a sufficiently **long clock period**.

Minimum clock period

DEF: The **minimum clock period** of a synchronous circuit C is the shortest clock period for which the timing constraints of the output signals and signals that feed the flip-flops are satisfied.

We denote the minimum clock period of a synchronous circuit by $\varphi^*(C)$.

- Minimum clock period does not exist if timing constraints are infeasible.
- “timing constraints are satisfied” - for every value of the delays provided that they are in their range. (i.e. actual propagation delay of λ is in $[0, pd(\lambda)]$.)
- if assumptions hold, then in canonic form

$$\varphi^*(C) = \max\{t_{pd}, pd(IN)\} + \max\{pd(\lambda), pd(\delta)\} + t_{su}.$$

Discussion

- The timing analysis of synchronous circuits in canonic form is overly pessimistic.
- The problem is that each of the combinational circuits λ and δ is regarded as a “gate” with a propagation delay.
- In practice it may be the case, for example, that the accumulated delay from the input IN to the output OUT is significantly different than the accumulated delay from S to the output OUT . The situation is even somewhat more complicated in the case of multi-bit signals.
- We now deal with the general case.


Initialization

We require that

$$[t_0 + t_{pd}, t_1 + t_{cont}] \subseteq \text{stable}(S)_0.$$

- after power-up, flip-flop output may be non-logical (and even meta-stable).
- solution: introduce a reset signal.
- boot-strapping problem: How is a reset signal generated?
- no solution to this problem within the digital abstraction (meta-stability). All we can try to do is reduce the probability of such an event.
- **reset controller** - a special circuit that generates a reset signal.

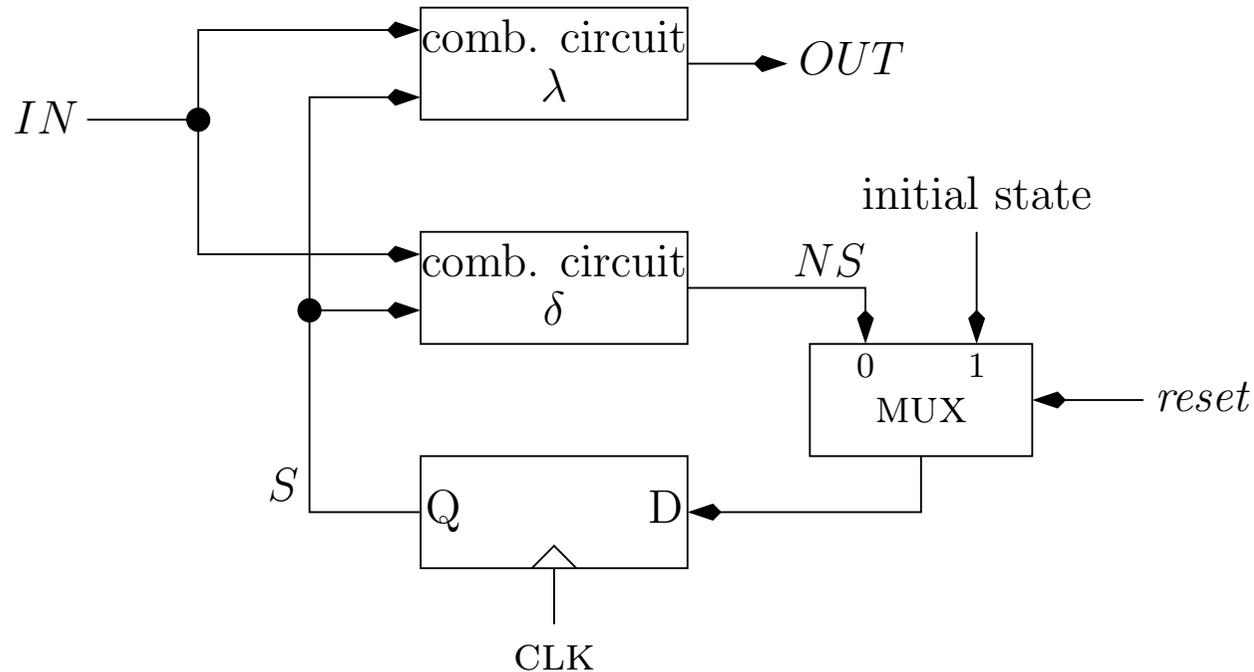Synchronous Circuit: canonic form with reset



Remark: NS may not be logical during reset.

Implementation of MUX must output initial-state if $reset = 1$.

Implementation based on drivers has this property, while implementation based on combinational gates may not have this property.

Functionality of Synchronous Circuits: canonic form

■ X_i - $dig(X)$ during $stable(X)_i$.

■ Assumptions:

$$cont(IN) \geq t_{cont}$$

$$hold(OUT) \leq t_{hold}$$

$$[t_0 + t_{pd}, t_1 + t_{cont}] \subseteq stable(S)_0,$$

$$\varphi(\text{CLK}) \geq \max\{t_{pd}, pd(IN)\} + \max\{pd(\lambda), pd(\delta)\} + t_{su},$$

CORO: Assumptions $\Rightarrow \forall i \geq 0$:

$$NS_i = \delta(IN_i, S_i)$$

$$OUT_i = \lambda(IN_i, S_i)$$

$$S_{i+1} = NS_i.$$

Finite State Machines

Corollary states that synchronous circuits implement **finite state machines**.

DEF: A **finite state machine** (FSM) is a 6-tuple $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, where

- Q is a set of **states**.
- Σ is the alphabet of the input.
- Δ is the alphabet of the output.
- $\delta : Q \times \Sigma \rightarrow Q$ is a **transition function**.
- $\lambda : Q \times \Sigma \rightarrow Q$ is an **output function**.
- $q_0 \in Q$ is an **initial state**.

Definition of FSM: remarks

- Other terms for a finite state machine are a **finite automaton with outputs**, **transducer**, and **Mealy Machine**.
- **Moore Machine** - an FSM in which the output function $\lambda : Q \rightarrow \Delta$.

What does an FSM do?

- abstract machine that operates as follows.
- input sequence $\{x_i\}_{i=0}^{n-1}$ of symbols over alphabet Σ .
- output sequence $\{y_i\}_{i=0}^{n-1}$ of symbols over alphabet Δ .
- sequence of states $\{q_i\}_{i=0}^n$. The state q_i is defined recursively:

$$q_{i+1} \triangleq \delta(q_i, x_i)$$

- The output y_i is defined as follows:

$$y_i \triangleq \lambda(q_i, x_i).$$

State Diagrams

FSMs are often depicted using state diagrams.


DEF: The **state diagram** corresponding to an FSM \mathcal{A} is a directed graph $G = (V, E)$ with edge labels $(x, y) \in \Sigma \times \Delta$. The vertex set V equals the state set S . The edge set E is defined by

$$E \triangleq \{(q, \delta(q, x)) : q \in Q \text{ and } x \in \Sigma\}.$$

An edge $(q, \delta(q, x))$ is labeled $(x, \lambda(q, x))$.

State Diagram: example

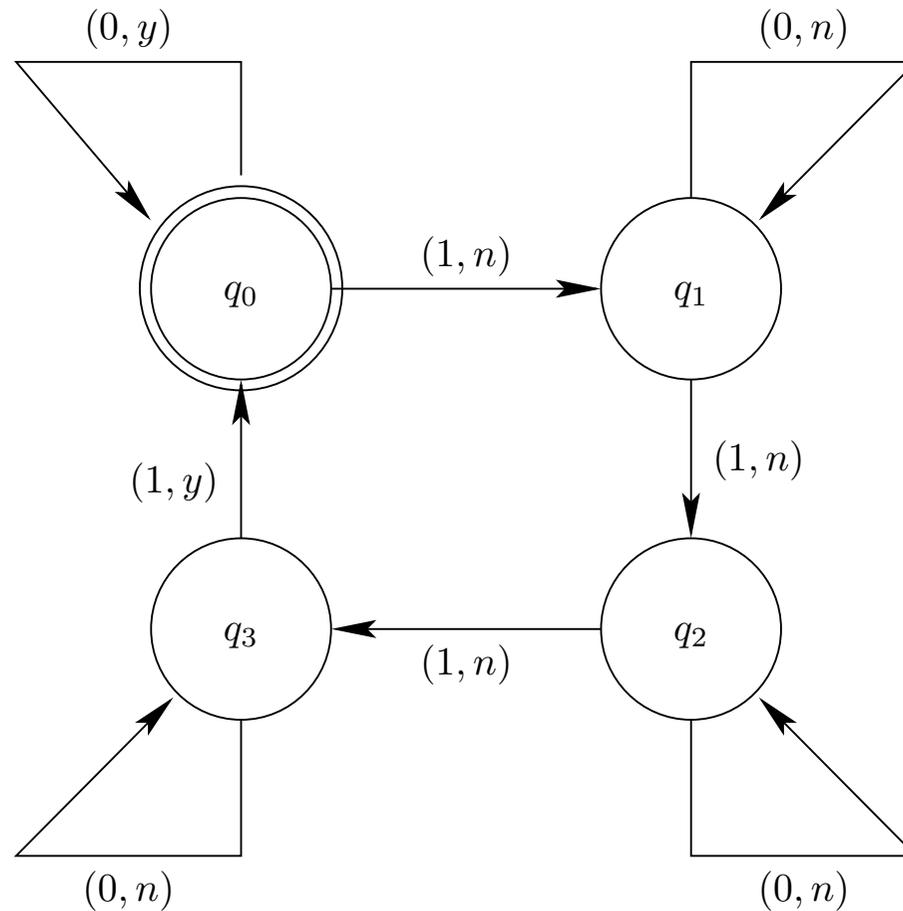A state diagram of an FSM that outputs y if the weight of the input so far is divisible by 4, and n otherwise.



Timing analysis: the general case

- Deal with a synchronous circuit that is not in canonic form.
- Algorithm that computes the minimum clock period $\varphi^*(C)$. (if timing constraints are feasible.)
- Algorithm that decides whether the timing constraints are feasible (i.e. conditions used by this algorithm are less restrictive than the conditions used in previous claims).

Review of timing constraints

Input constraints: For every input signal IN , guaranteed:

$$[t_i + pd(IN), t_{i+1} + cont(IN)] \subseteq stable(IN)_i.$$

Output constraints: For every output signal OUT , require:

$$[t_{i+1} - setup(OUT), t_{i+1} + hold(OUT)] \subseteq stable(OUT)_i.$$

Critical segments: For every signal NS that feeds a D -port of a flip-flop, require:

$$C_{i+1} \subseteq stable(NS)_i.$$

Algorithm: minimum clock period

- $C' \leftarrow$ combinational circuit obtained by stripping away flip-flops from C .
- For every gate v of C' define $d(v)$ as follows:

$$d(v) \triangleq \begin{cases} pd(IN) & \text{if } v \text{ feeds input signal } IN. \\ t_{pd} & \text{if } v \text{ corresponds to a } Q\text{-port.} \\ setup(OUT) & \text{if } v \text{ is fed by } OUT. \\ t_{su} & \text{if } v \text{ corresponds to a } D\text{-port.} \\ pd(v) & \text{if } v \text{ is a combinational gate of } C. \end{cases}$$

- Let $DG(C')$ denote the directed acyclic graph (DAG) that corresponds to C' . Let p' denote the longest path in $DG(C')$ with respect to the delays $d(v)$. Return $d(p')$.

Algorithm: correctness

define delays $c(v)$ to non-sink vertices in $DG(C')$ as follows.

$$c(v) \triangleq \begin{cases} cont(IN) & \text{if } v \text{ feeds an input signal } IN. \\ t_{cont} & \text{if } v \text{ corresponds to a } Q\text{-port of a flip-flop.} \\ cont(v) & \text{if } v \text{ is a combinational gate in } C. \end{cases}$$

Lemma: Consider a combinational gate, an input gate, or a flip-flop v in the synchronous circuit C . Let \mathcal{P}_v denote the set of all directed paths in the directed acyclic graph $DG(C')$ that begin at a source and end in v . If the output of every flip-flop is stable in the interval $[t_i + t_{pd}, t_{i+1} + t_{cont}]$, then every output N of v satisfies

$$[t_i + \max_{p \in \mathcal{P}_v} d(p), t_{i+1} + \min_{p \in \mathcal{P}_v} c(p)] \subseteq \mathbf{stable}(N)_i.$$

proof: $[t_i + \max_{p \in \mathcal{P}_v} d(p), t_{i+1} + \min_{p \in \mathcal{P}_v} c(p)] \subseteq \text{stable}(N)_i$.

- $\{v_0, \dots, v_{n-1}\}$ - topological sort of vertices of $DG(C')$.
- Let $v = v_j$. Proof by induction on j .
- Basis: two cases: (i) If v is an input gate, then input constraint. (ii) If v is a flip-flop, then assumption on the output of flip-flops.
- Step: same as basis if v is an input gate or a flip flop.
- Assume v is a combinational gate.
- Ind. Hyp. : every input N' of v_{j+1} satisfies equation.
- \Rightarrow every output N of v_{j+1} satisfies: (i) N becomes stable at most $d(v_{j+1})$ time units after its last input becomes stable, and (ii) N remains stable at least $c(v_{j+1})$ time units after its first input becomes instable.

Algorithm: correctness (cont.)

Claim: Suppose that: (i) for every signal fed by a Q -port of a flip-flop, $[t_i + t_{pd}, t_{i+1} + t_{cont}] \subseteq \text{stable}(S)_i$, (ii) for every input IN , $\text{cont}(IN) \geq t_{cont}$, and (iii) for every output OUT , $\text{hold}(OUT) \leq t_{hold}$. Then,

1. For every clock period $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$, the signals feeding D -ports of flip-flops are stable during the critical segment C_{i+1} .
2. For every clock period $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$, the output timing constraints corresponding to cycle i are satisfied.
3. For every clock period $\varphi(\text{CLK}) < \varphi^*(\text{CLK})$, a violation of the timing constraints is possible.

Proof: $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$ satisfies timing constraints

Let N denote signal that feeds a D -port of a flip-flop v that is fed by u . By Lemma, N is stable during the interval

$$[t_i + \max_{p \in \mathcal{P}_u} d(p), t_{i+1} + \min_{p \in \mathcal{P}_u} c(p)].$$

Since $\varphi(\text{CLK}) \geq \max_{p \in \mathcal{P}_v} d(p) = d(v) + \max_{p \in \mathcal{P}_u} d(p)$ and $d(v) = t_{su}$, we conclude that

$$t_{i+1} - t_i = \varphi(\text{CLK}) \geq t_{su} + \max_{p \in \mathcal{P}_u} d(p).$$

\Rightarrow signal N stable starting at

$$t_i + \max_{p \in \mathcal{P}_u} d(p) \leq t_{i+1} - t_{su}.$$

\Rightarrow setup-time constraint is satisfied.

Proof: $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$ - cont.

N is stable until $t_{i+1} + \min_{p \in \mathcal{P}_u} c(p)$.

However, every path $p \in \mathcal{P}_u$ begins at a source. A source may correspond to an input gate in C or a Q -port of a flip flop. Since $\text{cont}(IN) \geq t_{\text{cont}}$, we conclude that $c(s) \geq t_{\text{cont}}$, for every source s .

It follows that

$$\min_{p \in \mathcal{P}_u} c(p) \geq t_{\text{cont}} > t_{\text{hold}}.$$

Lemma: N is stable until $t_{i+1} + \min_{p \in \mathcal{P}_u} c(p) \geq t_{i+1} + t_{\text{hold}}$.
 \Rightarrow hold-time constraint is satisfied.

$\Rightarrow N$ is stable during the critical segment C_{i+1} , as required.

Proof: $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$ - cont.

Proof for an output signal *OUT* is similar.

Proof: $\varphi(\text{CLK}) < \varphi^*(\text{CLK}) \Rightarrow$ **violation**

- p - longest path in $DG(C')$ with respect to lengths $d(v)$. (p begins at a source and ends in a sink v .)
- Let p' denote the path obtained from p by omitting the sink v . It follows that

$$t_i + d(p') > t_{i+1} - d(v).$$

- If the actual propagation delays along p are maximal, then the signal feeding v is not stable at time $t_{i+1} - d(v)$.
- If v is a flip-flop, then its input is not stable during the critical segment.
- If v is an output gate, then its input does not meet the output constraint. The claim follows.

Corollary

If the circuit is properly initialized, then the clock period computed by the algorithm is the shortest clock period that satisfies all the timing constraints for all clock cycles i , for $i \geq 0$.

Formally...

Corollary - formal

CORO: Suppose that: (i) for every signal S fed by a Q -port of a flip-flop, $[t_0 + t_{pd}, t_1 + t_{cont}] \subseteq \text{stable}(S)_0$, (ii) for every input IN , $\text{cont}(IN) \geq t_{cont}$, and (iii) for every output OUT , $\text{hold}(OUT) \leq t_{hold}$. Then,

1. For every clock period $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$, the signals feeding D -ports of flip-flops are stable during every critical segment C_{i+1} , for $i \geq 0$.
2. For every clock period $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$, the output timing constraints corresponding to cycle i are satisfied, for every $i \geq 0$.
3. For every clock period $\varphi(\text{CLK}) < \varphi^*(\text{CLK})$, a violation of the timing constraints is possible.

Proof: Proof is by induction on the clock cycle i . □

Algorithm: feasibility of timing constraints

- So far, reasonable assumptions are made so that it is guaranteed that a minimum clock period exists.
- It is possible that these assumptions do not hold although the timing constraints are feasible.
- We now present an algorithm that verifies whether the timing constraints are feasible without relying on any assumptions.

Follow recipe of the lemma

Lemma states that, for every non-sink v in C' , the guaranteed stability interval of the signals that are output by v is:

$$[t_i + \max_{p \in \mathcal{P}_v} d(p), t_{i+1} + \min_{p \in \mathcal{P}_v} c(p)].$$

The $\varphi^*(C)$ algorithm deals with making sure that each such interval does not start too late (i.e. satisfy setup-time constraint).

Feasibility means checking that stability intervals do not end too early (i.e. satisfy hold-time constraint).

Follow recipe of the lemma - cont

Recall: signal fed by v is stable during

$$\left[t_i + \max_{p \in \mathcal{P}_v} d(p), t_{i+1} + \min_{p \in \mathcal{P}_v} c(p) \right].$$

Check that

1. For every u that feeds a D -port of a flip-flop, require

$$\min_{p \in \mathcal{P}_u} c(p) \leq t_{hold}.$$

2. For every u that feeds an output signal OUT , require

$$\min_{p \in \mathcal{P}_u} c(p) \leq hold(OUT).$$

violation \Rightarrow timing constraints are infeasible.

no violation \Rightarrow timing constraints are feasible.

Algorithmic Aspect

- All we need to check if timing constraints are feasible is to compute

$$\forall \text{ non-sink } v : \min_{p \in \mathcal{P}_v} c(p).$$

- Compute shortest path in a DAG (can be done in linear time using depth first search).
- After these values are computed for all the non-sinks, the algorithm simply checks hold-time constraints for every D -port and for every output.
- If a violation is found, then the timing constraints are infeasible.

Recap

- We started with a syntactic definition of a synchronous circuit.
- We then attached timing constraints to the inputs and outputs of synchronous circuit.
- For a given synchronous circuit C with input/output timing constraints, we differentiate between two cases:
 - timing constraints are infeasible \Rightarrow cannot guarantee well defined functionality of C . For example, if the timing constraints are not met, then inputs of flip-flops might not be stable during the critical segments, and then the flip-flop output is not guaranteed to be even logical.
 - timing constraints are feasible \Rightarrow functionality is well defined provided that the clock period satisfies $\varphi(\text{CLK}) \geq \varphi^*(\text{CLK})$.

Functionality

- Assume that the timing constraints are feasible.
- Introduce a trivial timing model called the **zero delay model**.
- In this model, time is discrete and in each clock cycle, the circuit is reduced to a combinational circuit.
- Advantage: decouple timing issues from functionality and enables simple logical simulations.

The zero delay model

- In the zero delay model we assume that all the parameters of all the components are zero (i.e. $t_{su} = t_{hold} - t_{cont} = t_{pd} = 0$, $pd(IN) = cont(IN) = setup(OUT) = hold(OUT) = 0$, and $d(G) = 0$, for every combinational gate G). Under this unrealistic assumption, the timing constraints are feasible.
- By Lemma, it follows that, in the zero delay model, the stability interval of every signal is $[t_i, t_{i+1})$.
- Following Corollary (synchronous circuit implements an FSM), we conclude that, for every signal X , X_i is well defined.

Simulation of a synchronous circuit

Simulation during cycles $i = 0, \dots, n - 1$ in the zero propagation model proceeds as follows:

assume: flip-flops are initialized (\vec{S}_0 - initial values of FFs).

1. Construct comb. circuit C' that corresponds to C .
2. For $i = 0$ to $n - 1$ do:
 - (a) Simulate C' with input values \vec{S}_i and $I\vec{N}_i$.
 - (b) For every output OUT^j , let y denote the value that is fed to y . We set $OUT_i^j = y$.
 - (c) For every D -port NS^j of a flip-flop, let y denote the value that is fed to the flip-flop. We set $NS_i^j = y$.
 - (d) For every Q -port S^j of a flip-flop, define $S_{i+1}^j \leftarrow NS_i^j$, where NS^j denotes the signal that feeds the D -port of the flip-flop.

Summary

- define synchronous circuits.
- canonic form of synchronous circuits:
 - definition of timing constraints.
 - formulation of sufficient conditions for satisfying the timing constraints.
 - simplify sufficient conditions by relying on the assumption that the input originates from a flip-flop and the output is eventually fed to a flip-flop.
 - define the minimum clock period.
 - initialization.
 - synchronous circuit implement FSMs.

Summary -cont.

- general case of synchronous circuits (not in canonic form).
 - algorithm: min. clock period.
 - algorithm: feasibility of timing constraints.
- Functionality:
 - zero delay model.
 - simulation.