

## Introduction to Digital Computers - Fall 1997

### Assignment No. 3

Course homepage: [http://www.eng.tau.ac.il/~guy/Digital\\_Computers/dc\\_home.html](http://www.eng.tau.ac.il/~guy/Digital_Computers/dc_home.html)

#### Deadline: March 29th

1. Define a ripple carry adder (RCA) of  $n$  bits. Prove its correctness. Write the (closed - not recurrence) equations for its delay and cost.
2. Consider a situation in which an  $n$ -bit adder of unsigned binary strings has only the outputs: sum  $s \in \{0, 1\}^n$ , and carry-out bit  $c_n \in \{0, 1\}$ .

A two's complement adder requires the carry-bit  $c_{n-1}$  to generate the *ovf* signal.

Show how an  $(n + 1)$ -bit adder of unsigned binary strings can be used to construct an  $n$ -bit two's complement adder. Prove the correctness of your design.

3. Prove that the following operator  $*$  :  $\Sigma \times \Sigma \rightarrow \Sigma$ , where  $\Sigma = \{0, 1, 2\}$ , is associative.

$*$	2	1	0
2	2	2	2
1	2	1	0
0	0	0	0

Why is the associativity of the operator  $*$  required for the correctness of a parallel prefix circuit  $PPC(n)$ ?

4. Suggest three different encodings of  $\Sigma = \{0, 1, 2\}$  using bits. For every encoding suggest a  $*$ -gate and formulate the cost and delay of an adder based on a  $CLA(n)$ . Compute the cost and delay for  $n = 8, 16, 32, 64, 128$ , and compare the encodings.
5. Draw a parallel prefix circuit  $PPC(16)$  using only  $*$ -gates.
6. Design a circuit in which every prefix  $x_i * x_{i-1} * \dots * x_0$  is computed using a separate circuit. Write the cost and delay equations of your design. Compare them with those of  $PPC(n)$ .